

---

## ECE241, PRA0105 - Digital Logic

Name: Christina Pizzonia  
Student Number: 1007914250


Due Date: 19 September, 2023  
Prelab: Number 1

---

### Part I
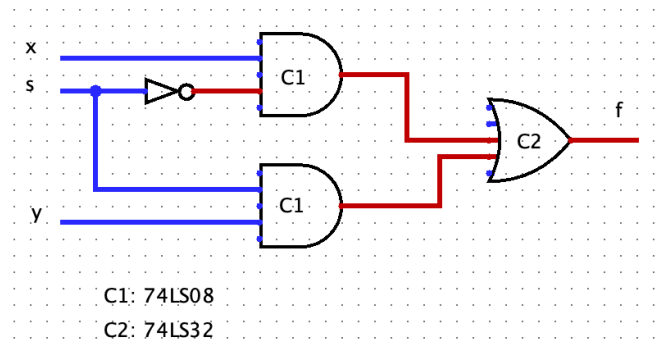
#### 1. Multiplexer schematic diagram

This diagram illustrates the resultant function  $f = \bar{s}x + xy$ . Note:




- 7404: Not
- 7408: And
- 7432: Or

#### 2. Truth table

x	s	y	$f = x\bar{s} + ys$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1
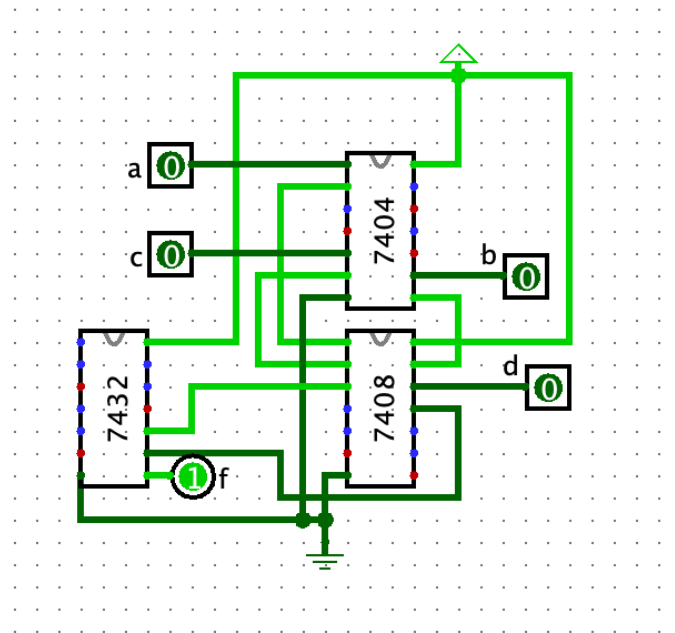
### 3. Logisim schematic and simulation output



Combinational Analysis

Inputs

Outputs

Table

Expression

Minimized

a	b	c	d	f
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

Build Circuit

#### 4. Cheaper implementation

No, there is no cheaper implementation (i.e. expression cannot be simplified using Boolean algebra).

## **Part II**

### **6. Simpler implementation**

#### **1. Schematic**

#### **2. Truth table**

#### **3. Logisim schematic and simulation output**